
FREE LEARNING RESOURCE

Introduction to Motor Control

A beginner-friendly guide to understanding how motor control works

A beginner-friendly introduction for electricians and technicians who understand basic electricity but are new to motor control.

AUTHOR

Isah The Technician

WEBSITE

<https://isah.online>

Contents

01	Introduction
02	What Is an Electric Motor?
03	Why Do We Need Motor Control?
04	Basic Motor Control Components
05	Basic Start and Stop Control
06	What Is a Contactor?
07	What Is an Overload Relay?
08	Basic Motor Control Circuit
09	Power Circuit vs Control Circuit
10	Common Motor Control Problems
11	A Simple Troubleshooting Method
12	Key Things to Remember
–	Quick Reference

01 Introduction

This guide is a simple introduction to motor control. It is written for people who understand basic electricity but are new to how motors are controlled in industrial and practical settings.

This is not an advanced manual. It is a starting point to help you understand the basic ideas before you move on to more advanced topics.

WHO THIS GUIDE IS FOR

This guide is for electrical apprentices, beginner technicians, students, and electricians who are entering industrial work for the first time.

02 What Is an Electric Motor?

An electric motor is a device that changes electrical energy into movement. Motors are used to drive machines such as conveyors, pumps, fans and mixers. When electrical power is supplied correctly, the motor turns and provides the movement needed to run the machine.

Most of the motors you will work with in industrial settings are AC motors, since AC power is the standard supply in homes and factories.

03 Why Do We Need Motor Control?

A motor cannot simply be connected straight to a power supply and left alone. We need motor control to:

- Safely start the motor.
- Stop the motor when needed.
- Protect the motor from damage caused by problems such as overload.

04 Basic Motor Control Components

Here are the basic components you will find in a motor control system.

MOTOR	The device that changes electrical energy into movement.
BREAKER	Protects the circuit by switching off when there is too much current.
ISOLATOR	Used to completely disconnect the circuit for maintenance.
CONTACTOR	A switch that turns the motor circuit on or off using an electromagnet.
OVERLOAD RELAY	Protects the motor by detecting too much current and stopping the circuit before the motor is damaged.
PUSH BUTTONS	Used by a person to start or stop the motor.
AUXILIARY CONTACTS	Extra contacts on a contactor used to hold the circuit on or send signals to other control devices.
INDICATOR LAMPS	Show the status of the motor, such as running, stopped or fault.

05 Basic Start and Stop Control

A basic start and stop control uses a few simple parts working together.

START PUSH BUTTON

When pressed, it sends power to the contactor coil to start the motor.

STOP PUSH BUTTON

When pressed, it breaks the circuit and stops the motor.

CONTACTOR COIL

When energized, it closes the main contacts and starts the motor.

HOLDING (AUXILIARY) CONTACT

Keeps the contactor energized after the start button is released, so the operator does not need to hold the button down.

These parts work together so the motor starts when the start button is pressed and keeps running until the stop button is pressed.

06 What Is a Contactor?

A contactor is an electrically operated switch. It uses a coil to create a magnetic field that closes its main contacts, allowing current to flow to the motor. Contactors are used for motor control because they can safely switch the higher current needed to run a motor.

Contactors come in different sizes depending on the size of the motor they control. Always check that a contactor is rated for the motor you are working with before it is used.

07 What Is an Overload Relay?

An overload relay protects the motor from damage. It monitors the current going to the motor. If the current becomes too high for too long, the overload relay trips and stops the circuit, protecting the motor from overheating and damage.

The overload relay is normally set based on the motor's rated current. This is why it helps to check the motor's nameplate details before the overload setting is adjusted.

08 Basic Motor Control Circuit

Below is a simple diagram of a basic start-stop control circuit. It shows how the stop button, start button, contactor coil and holding contact work together.

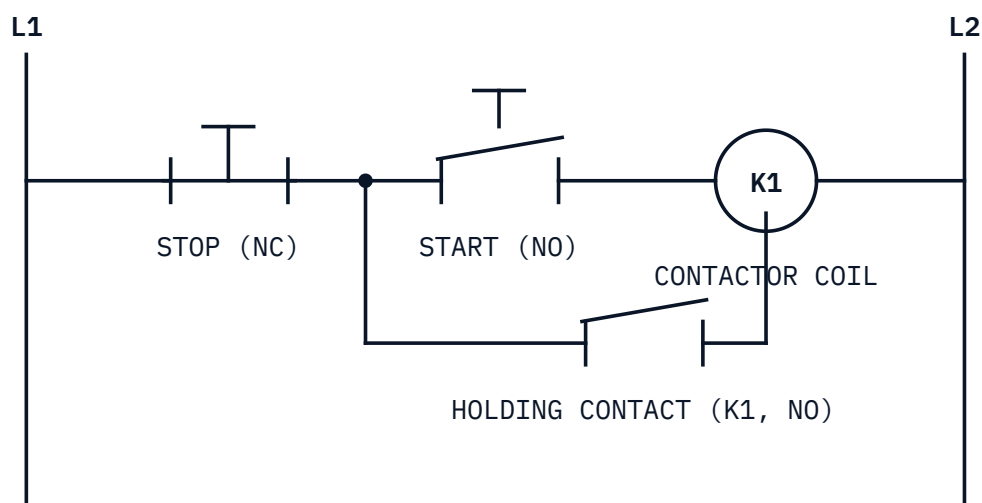


FIG. 1 – A simplified start-stop control circuit with a holding (auxiliary) contact.

When the start button is pressed, current flows through the stop button (which is normally closed) and the start button, energizing the contactor coil. This closes the main contacts and the holding contact. The holding contact then keeps the circuit closed even after the start button is released. Pressing the stop button breaks the circuit and de-energizes the coil, stopping the motor.

09 Power Circuit vs Control Circuit

A motor control system usually has two circuits.

HIGHER CURRENT

Power circuit

Carries the higher current that runs the motor itself. It usually includes the main contacts of the contactor and the wiring straight to the motor.

SMALLER CURRENT

Control circuit

Carries a smaller current used to control the contactor coil. It includes push buttons, auxiliary contacts and other control devices.

Understanding the difference helps you know where to check when troubleshooting a motor control problem. If the motor has no power at all, the fault is often in the power circuit. If the contactor will not energize, the fault is often in the control circuit.

10 Common Motor Control Problems

Motor does not start

could be a problem in the control circuit, power circuit, or a tripped overload.

Contactor does not energize

could mean no control voltage, a faulty push button, or a wiring problem.

Overload trips

could mean the motor is drawing too much current, or the overload setting is wrong.

Control voltage is missing

could mean a blown fuse or tripped breaker in the control circuit.

Loose connection

a loose wire can cause a motor to work sometimes and not other times.

11 A Simple Troubleshooting Method

Use this simple order when troubleshooting a motor control problem:

01 Observe

02 Check the supply

03 Check the control circuit

04 Check the contactor

05 Check protection

06 Test the motor

SAFETY

Always follow safe procedures. Isolate the power before any physical checks, and only take live measurements if you are trained and following the correct safety steps.

12 Key Things to Remember

- Motor control circuits protect and control the motor safely.
- The power circuit carries the higher current; the control circuit carries the smaller current for control devices.
- A contactor switches the motor on and off using an electromagnetic coil.
- An overload relay protects the motor from too much current.
- Understanding a simple start-stop circuit is the foundation for more advanced motor control.
- Always isolate power and follow safe procedures before checking or touching any part of the circuit.

Quick Reference

A short recap of the key terms from this guide, for a fast lookup.

CONTACTOR	Electrically operated switch that turns the motor circuit on or off.
OVERLOAD RELAY	Protects the motor by stopping the circuit if current is too high for too long.
POWER CIRCUIT	Carries the higher current that runs the motor.
CONTROL CIRCUIT	Carries the smaller current that controls the contactor coil.
HOLDING CONTACT	Keeps the contactor energized after the start button is released.
ISOLATOR	Disconnects the circuit completely for maintenance.

Motor control can look complicated at first, but it becomes clearer once you understand the basic parts and how they work together. Keep learning and keep practicing.

– Isah The Technician, isah.online